

# CS250P: Computer Systems Architecture

## Circuits Recap – Digital Why And How



Sang-Woo Jun

Fall 2023



Large amount of material adapted from MIT 6.004, “Computation Structures”,  
Morgan Kaufmann “Computer Organization and Design: The Hardware/Software Interface: RISC-V Edition”,  
and CS 152 Slides by Isaac Scherson

# Course outline

- ❑ Part 1: The Hardware-Software Interface
  - What makes a 'good' processor?
  - Assembly programming and conventions
- ❑ Part 2: Recap of digital design
  - Combinational and sequential circuits
  - How their restrictions influence processor design
- ❑ Part 3: Computer Architecture
  - Computer Arithmetic
  - Simple and pipelined processors
  - Caches and the memory hierarchy
- ❑ Part 4: Computer Systems
  - Operating systems, Virtual memory

“Complex ISA can slow down the clock”



Why?

# The digital abstraction

“Building Digital Systems in an Analog World”
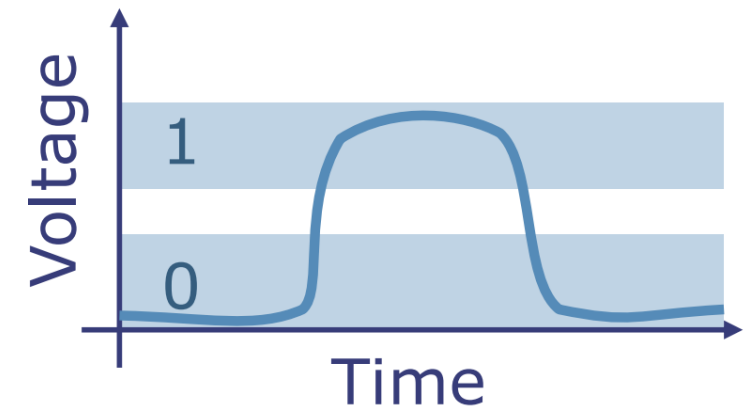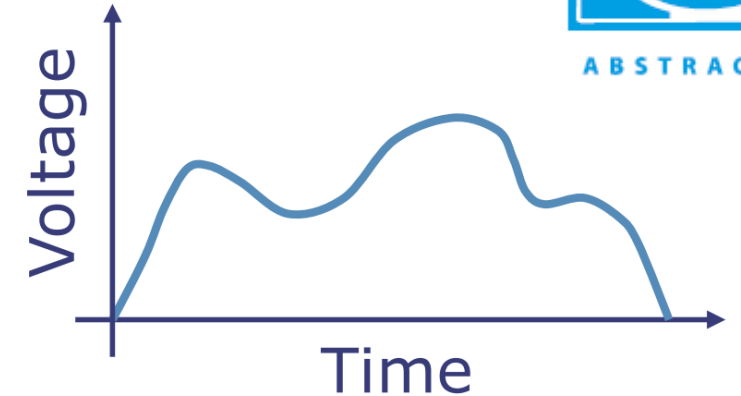
# The digital abstraction

- ❑ Electrical signals in the real world is analog
  - Continuous signals in terms of voltage, current,
- ❑ Modern computers represent and process information using discrete representations
  - Typically binary (bits)
  - Encoded using ranges of physical quantities (typically voltage)



# Aside: Historical analog computers


- ❑ Computers based on analog principles have existed
  - Uses analog characteristics of capacitors, inductors, resistors, etc to model complex mathematical formulas
    - Very fast differential equation solutions!
    - Example: Solving circuit simulation would be very easy if we had the circuit and was measuring it




Polish analog computer AKAT-1 (1959)

Source: Topory

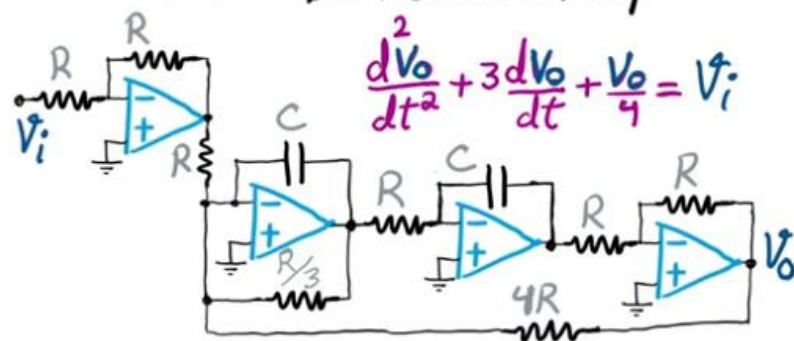Analog Computer: prove this circuit solves Differential equation




Differential Equation Solver

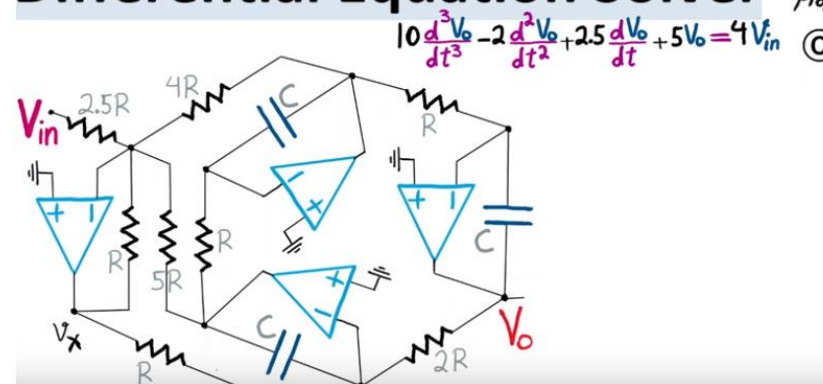

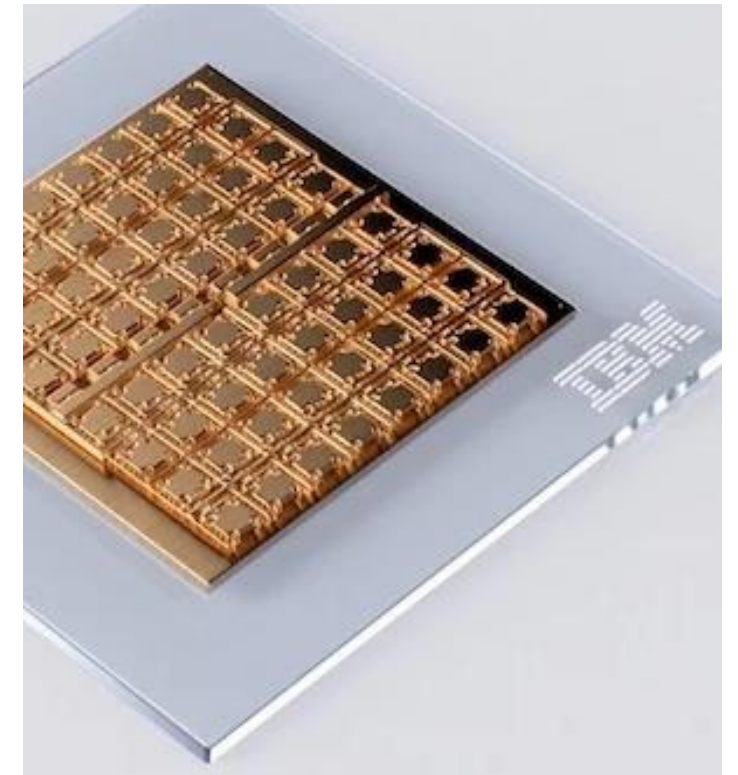
# Aside: Historical analog computers

- ❑ Some modern resurgence as well!
  - Research on sub-modules performing fast non-linear computation using analog circuitry

“A neural network layer can be implemented on (at least) one crossbar, in which the weights of that layer are stored in the charge or conductance state of the memory devices at the crosspoints.”



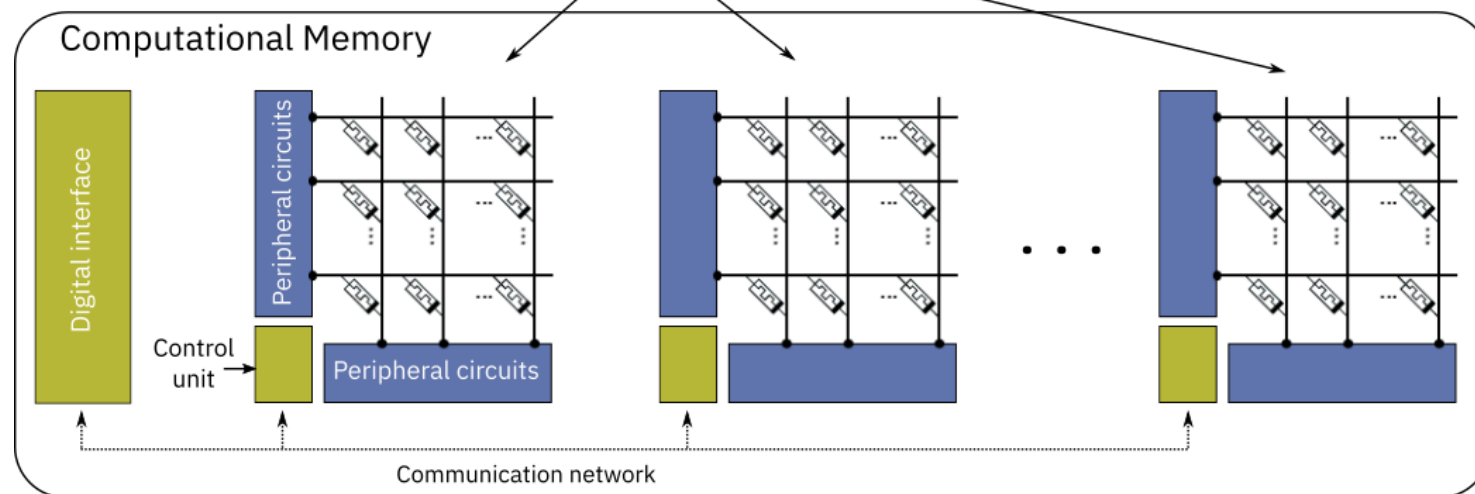“The IBM AI analog chip includes 64 analog tiles, each of which can be used as a layer in a neural network”



# Aside: Historical analog computers

Why are digital systems desirable?


**Emphasis: NOISE!!**



# Using voltage digitally
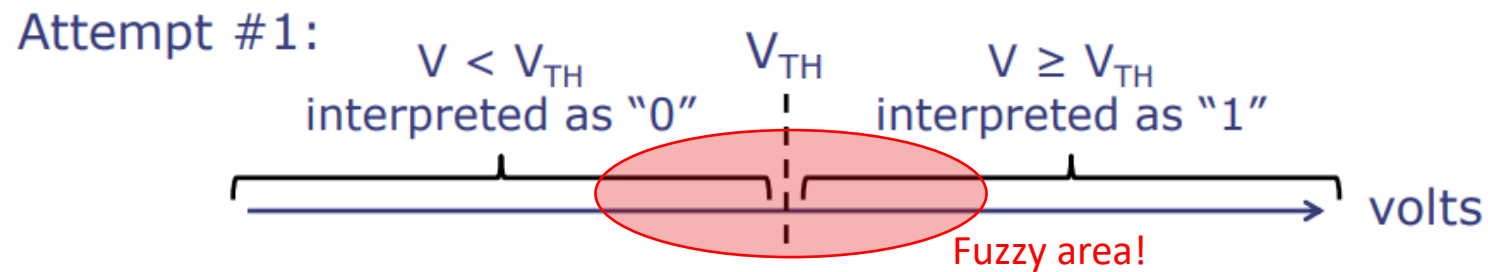
## □ Key idea

- Encode two symbols, “0” and “1” (1 bit) in an analog space
- And use the same convention for every component and wire in system





Problem: There is always noise between transmitter and receiver

Also, noise can accumulate as we pass through more gates



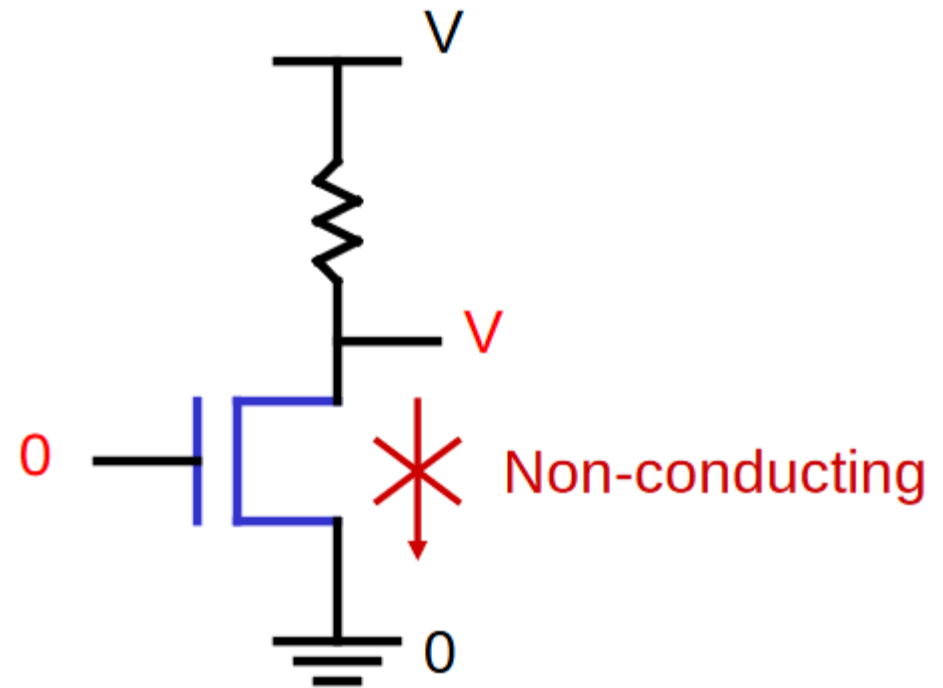
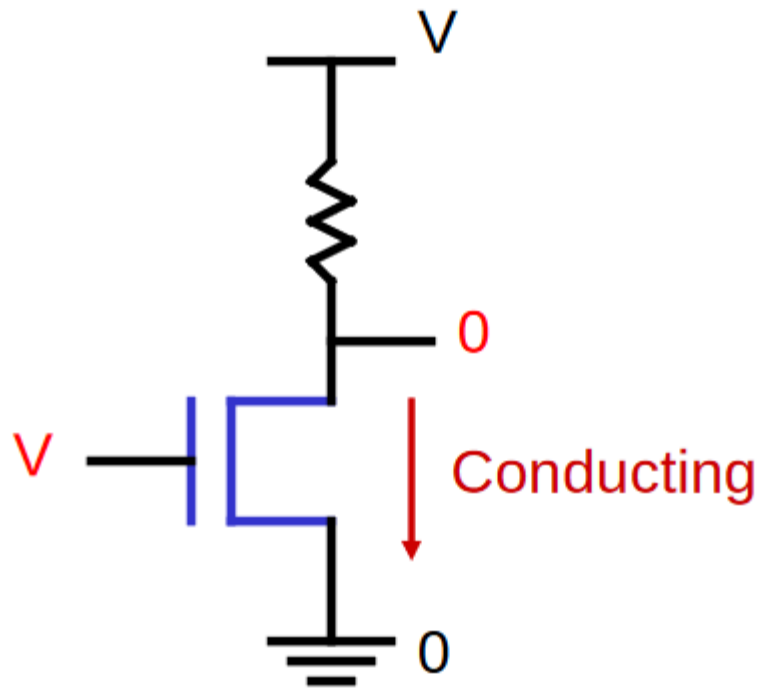
# Building block of digital design: Transistors

- A 3-terminal design which works as a switch




# Building block of digital design: Transistors

- Composed to create digital logic

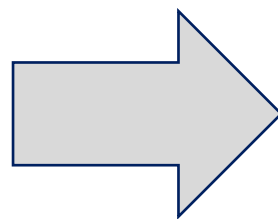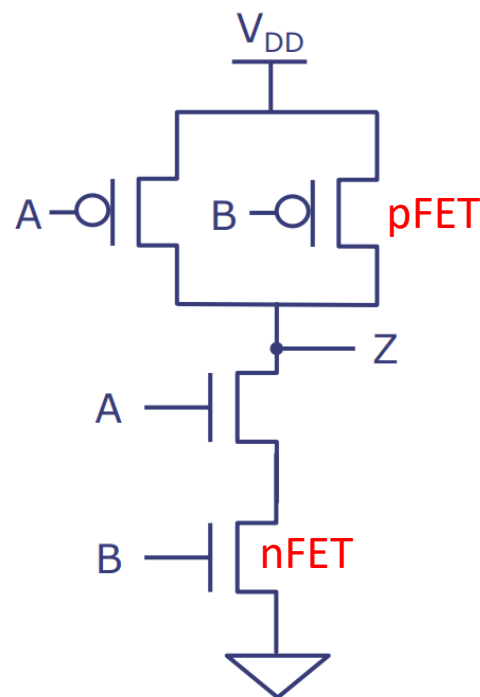

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0


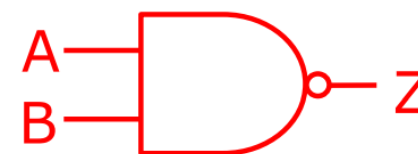


CMOS NAND Gate

# Using voltage digitally
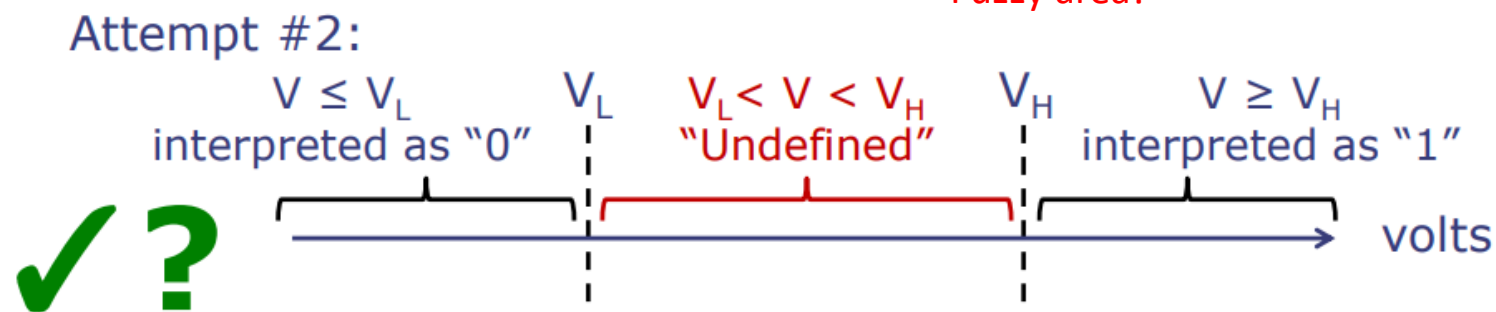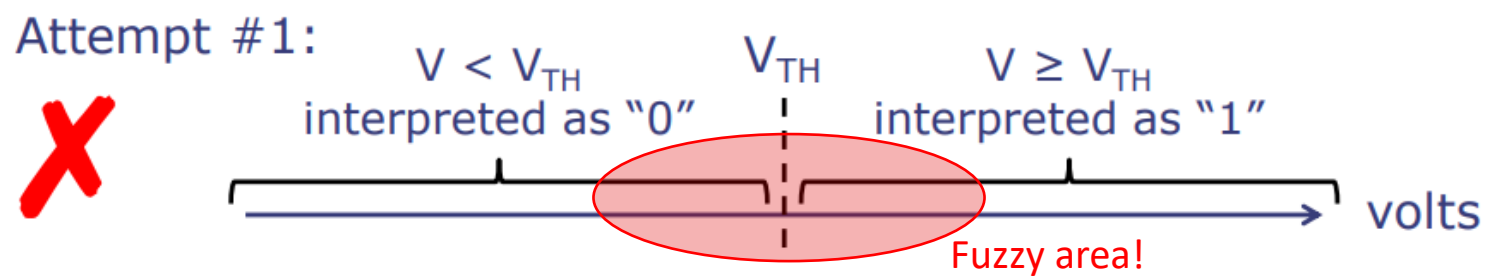
## □ Key idea


- Encode two symbols, “0” and “1” (1 bit) in an analog space
- And use the same convention for every component and wire in system



$V_L$  and  $V_H$  of output are enforced during component design and manufacture
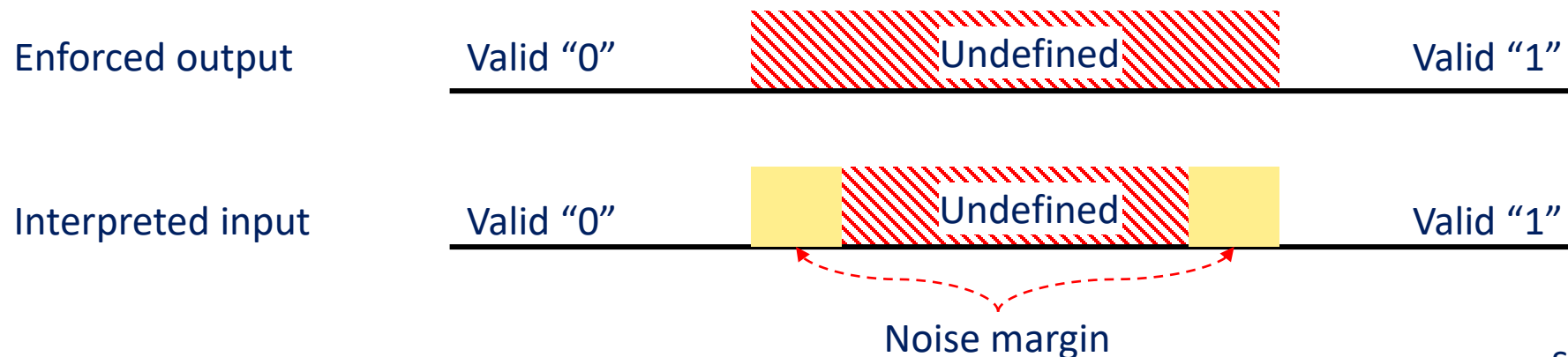
# Handling noise

- ❑ When a signal travels between two entities, **there will be noise**
  - Temperature, electromagnetic fields, interaction with surrounding modules, ...
- ❑ What if  $V_{out}$  is barely lower than  $V_L$ , or barely higher than  $V_H$ ?
  - Noise may push the signal into invalid range
  - Rest of the system runs into undefined state!
- ❑ Solution: Output signals use a stricter range than input



# Voltage Transfer Characteristic

## ❑ Example component: Buffer


- A simple digital device that copies its input value to its output

## ❑ Voltage Transfer Characteristic (VTC):

- Plot of  $V_{out}$  vs.  $V_{in}$  where each measurement is taken after any transients have died out.
- Not a measure of circuit speed!
  - Only determines behavior under static input
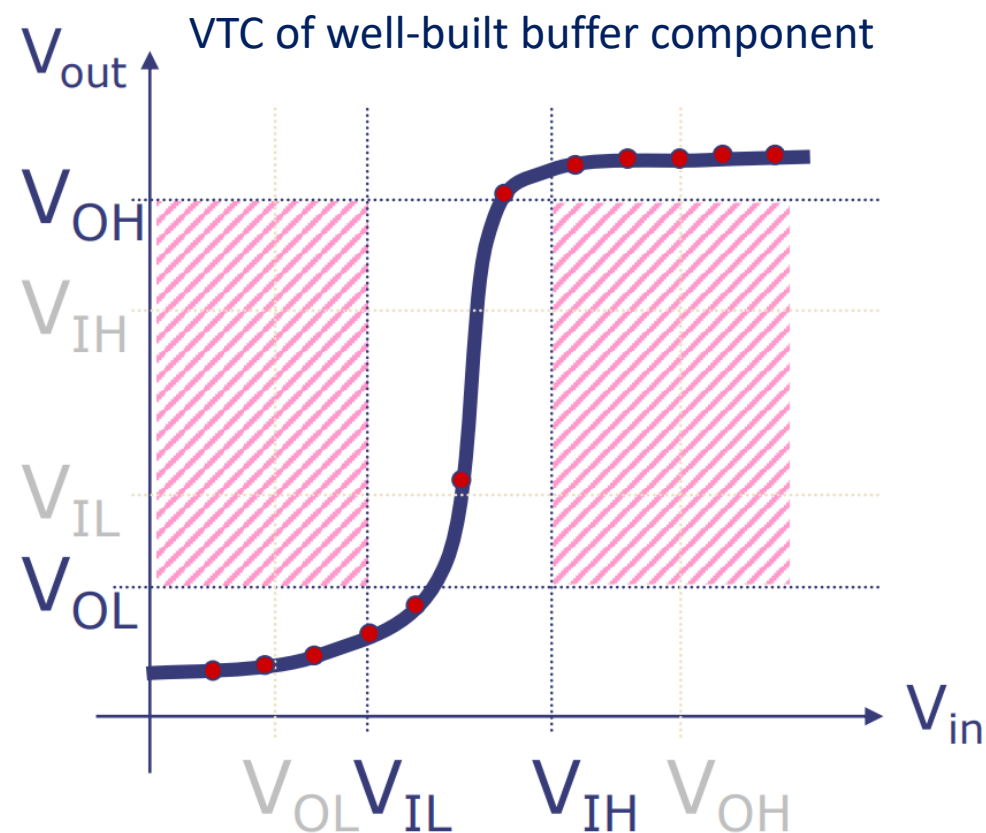
## ❑ Each component generates a new, “clean” signal!


- Noise from previous component corrected


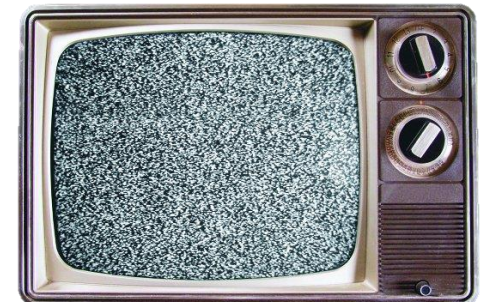
# Benefits of digital systems



- ❑ Digital components are “restorative”
  - Noise is cancelled at each digital component
  - Very complex designs can be constructed on the abstraction of digital behavior
- ❑ Compare to analog components
  - Noise is accumulated at each component
  - Lay example: Analog television signals! (Before 2000s)
    - Limitation in range, resolution due to transmission noise and noise accumulation
    - Contrary: digital signals use repeaters and buffers to maintain clean signals



# CS250P: Computer Systems Architecture

## Digital Circuit Design Recap



Sang-Woo Jun

Fall 2023




Large amount of material adapted from MIT 6.004, “Computation Structures”,  
Morgan Kaufmann “Computer Organization and Design: The Hardware/Software Interface: RISC-V Edition”,  
and CS 152 Slides by Isaac Scherson


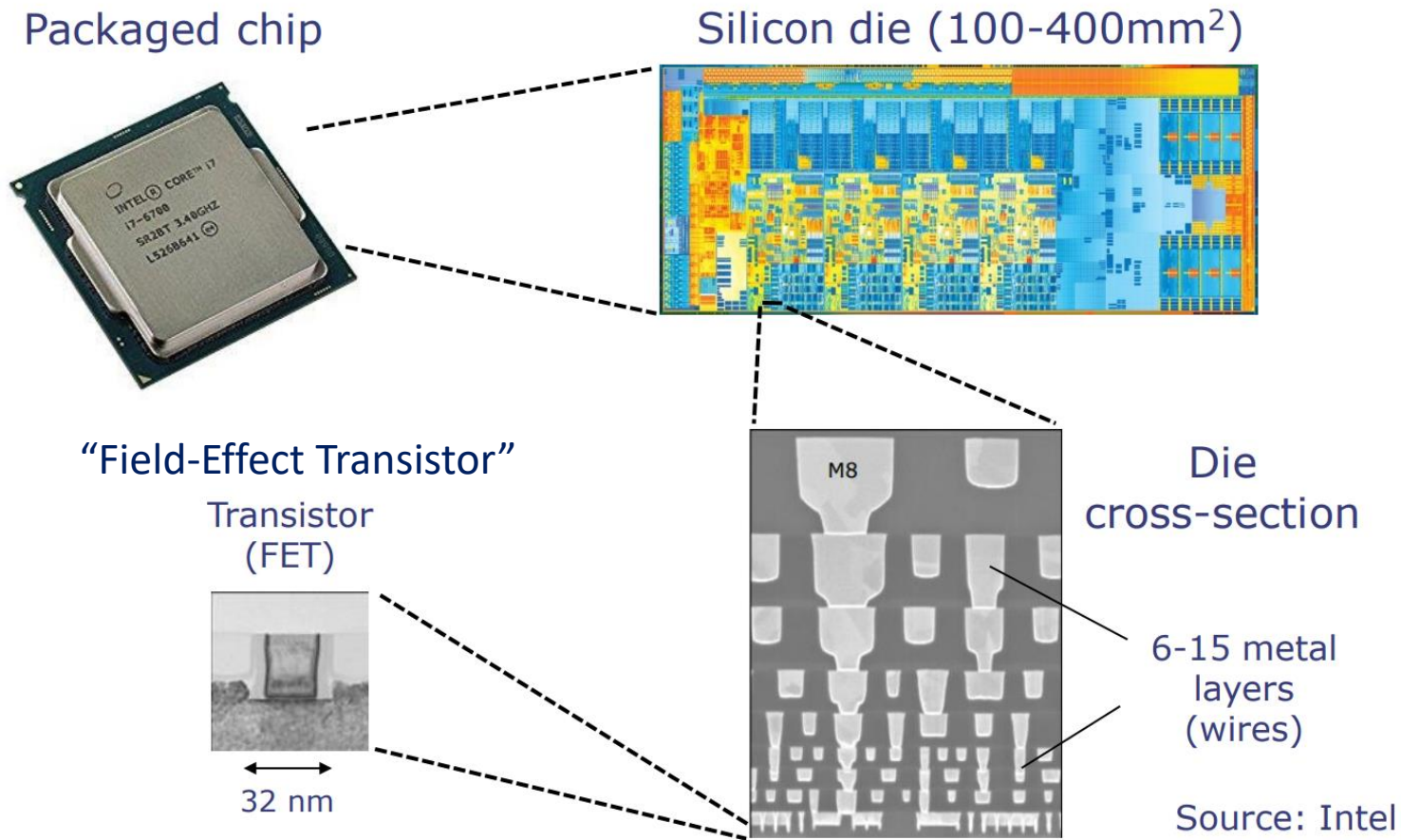
# The basic building block: CMOS transistors



(“Complementary Metal–Oxide–Semiconductor”)




Everything is built as a network of transistors!
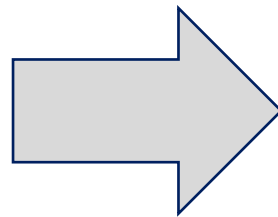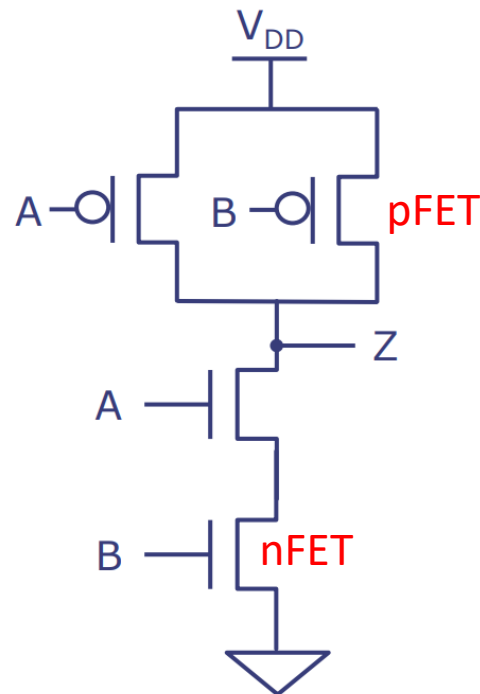
# The basic building block: CMOS FETs

- Remember CS151 – FETs come in two varieties, and are composed to create Boolean logic




A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

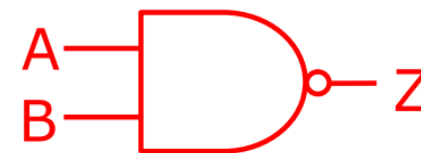

CMOS NAND Gate

# Making chips out of transistors...?

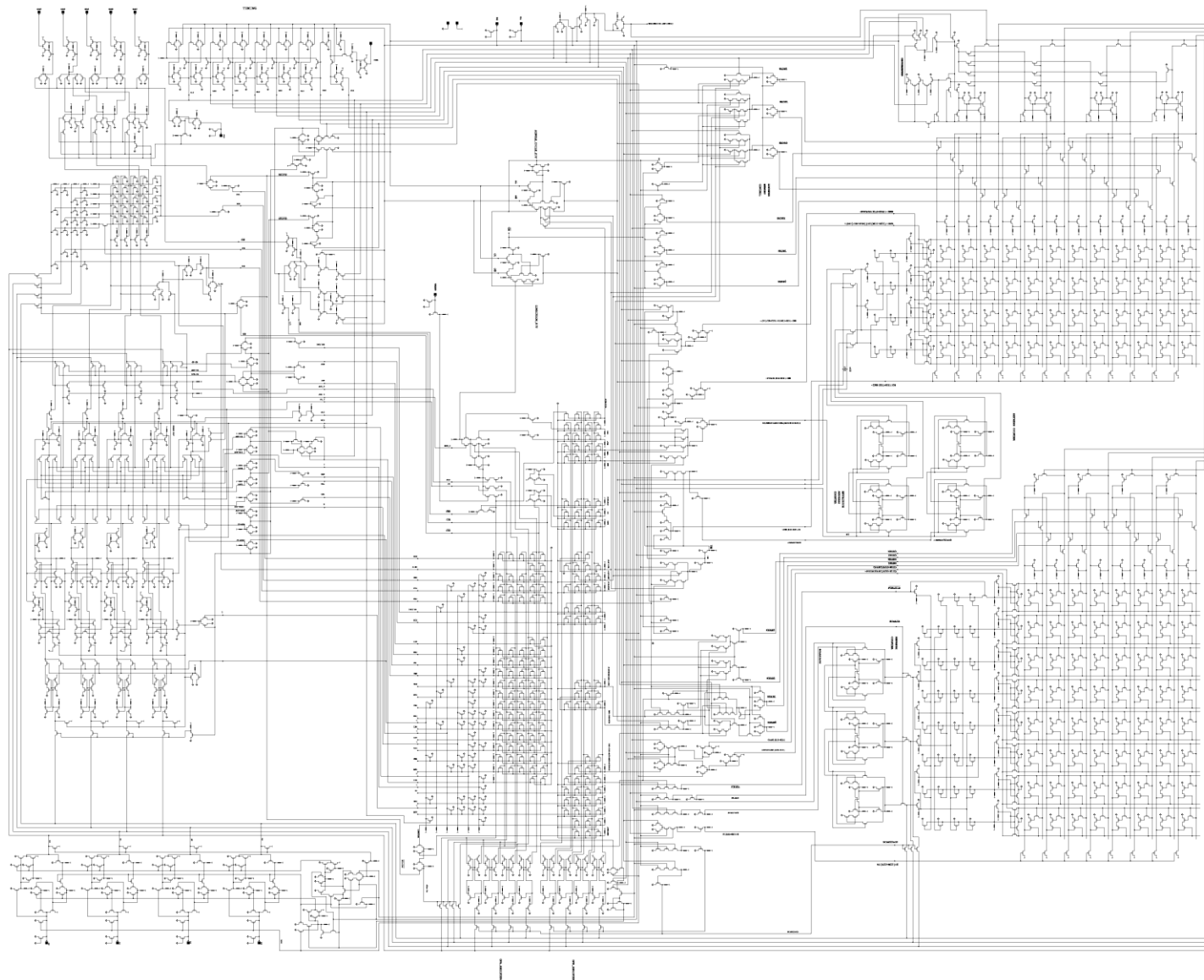

Intel 4004 Schematics  
drawn by Lajos Kintli and Fred Huettig  
for the Intel 4004 50<sup>th</sup> anniversary project

# The basic building block 2: Standard cell library

## □ Standard cell

- Group of transistor and interconnect structures that provides a boolean logic function
  - Inverter, buffer, AND, OR, XOR, ...

- For a specific implementation technology/vendor/etc...
- Also includes physical characteristic information

## □ Eventually, chips designs are expressed as a group of standard cells networked via wires

- Among what is sent to a fab plant

Gate	Delay (ps)	Area ( $\mu^2$ )
<b>Inverter</b>	20	10
<b>Buffer</b>	40	20
<b>AND2</b>	50	25
<b>NAND2</b>	30	15
<b>OR2</b>	55	26
<b>NOR2</b>	35	16
<b>AND4</b>	90	40
<b>NAND4</b>	70	30
<b>OR4</b>	100	42
<b>NOR4</b>	80	32

Example:

Various components have different delays and area!

The actual numbers are not important right now

# Aside: Describing chips for foundries

- ❑ GDSII, OASIS file formats
- ❑ Depicts many standard cells connected via multiple wire layers

