

# CS152: Computer Systems Architecture

## Circuits Recap – Digital Why And How



Sang-Woo Jun

Spring 2023

# Course outline



- ❑ Part 1: The Hardware-Software Interface
  - What makes a 'good' processor?
  - Assembly programming and conventions
- ❑ Part 2: Recap of digital design
  - Combinational and sequential circuits
  - How their restrictions influence processor design
- ❑ Part 3: Computer Architecture
  - Computer Arithmetic
  - Simple and pipelined processors
  - Caches and the memory hierarchy
- ❑ Part 4: Computer Systems
  - Operating systems, Virtual memory

# The digital abstraction

“Building Digital Systems in an Analog World”
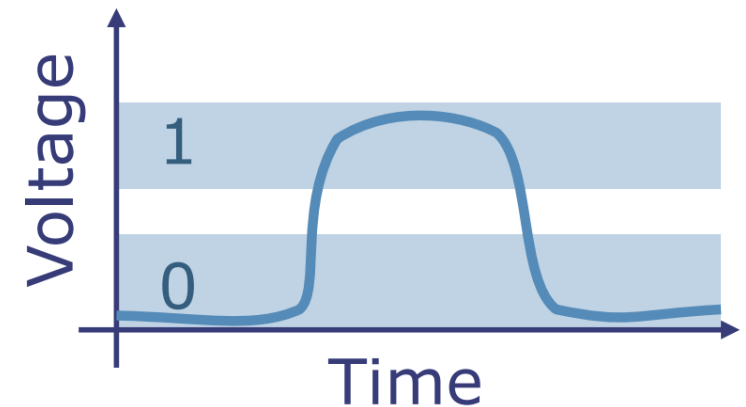 
# The digital abstraction

- ❑ Electrical signals in the real world is analog
  - Continuous signals in terms of voltage, current,
- ❑ Modern computers represent and process information using discrete representations
  - Typically binary (bits)
  - Encoded using ranges of physical quantities (typically voltage)




# Aside: Historical analog computers

- ❑ Computers based on analog principles have existed
  - Uses analog characteristics of capacitors, inductors, resistors, etc to model complex mathematical formulas
    - Very fast differential equation solutions!
    - Example: Solving circuit simulation would be very easy if we had the circuit and was measuring it
- ❑ Some modern resurgence as well!
  - Research on sub-modules performing fast non-linear computation using analog circuitry

Flash transistors can be modeled as **variable resistors** representing the weight

The  $V=IR$  current equation will achieve the math we need:  
Inputs (X) = DAC  
Weights (R) = Flash transistors  
Outputs (Y) = ADC Outputs

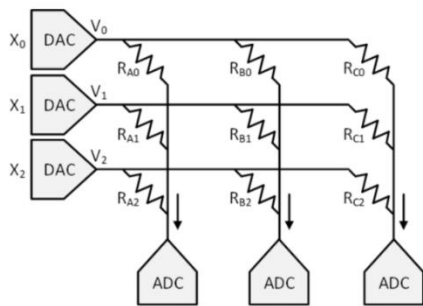The ADCs convert current to digital codes, and provide the non-linearity needed for DNN



Why are digital systems desirable?

Hint: Noise




Polish analog computer AKAT-1 (1959)  
Source: Topory

# Using voltage digitally
 
## □ Key idea

- Encode two symbols, “0” and “1” (1 bit) in an analog space
- And use the same convention for every component and wire in system



Problem: There is always noise between transmitter and receiver



Also, noise can accumulate as we pass through more gates



# Using voltage digitally
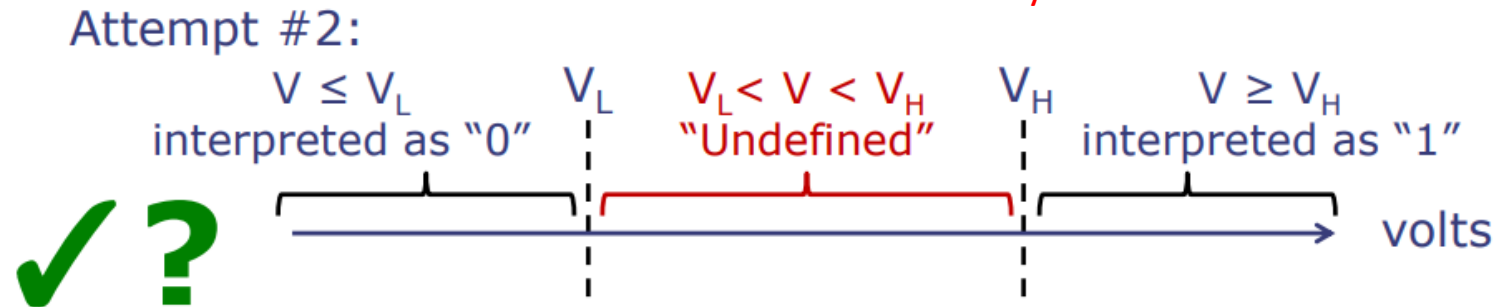 
## □ Key idea


- Encode two symbols, “0” and “1” (1 bit) in an analog space
- And use the same convention for every component and wire in system



$V_L$  and  $V_H$  of output are enforced  
during component design and manufacture
 
# Handling noise

- ❑ When a signal travels between two entities, **there will be noise**
  - Temperature, electromagnetic fields, interaction with surrounding modules, ...
- ❑ What if  $V_{out}$  is barely lower than  $V_L$ , or barely higher than  $V_H$ ?
  - Noise may push the signal into invalid range
  - Rest of the system runs into undefined state!
- ❑ Solution: Output signals use a stricter range than input





# Voltage Transfer Characteristic

## □ Example component: Buffer


- A simple digital device that copies its input value to its output

## □ Voltage Transfer Characteristic (VTC):

- Plot of  $V_{out}$  vs.  $V_{in}$  where each measurement is taken after any transients have died out.
- Not a measure of circuit speed!
  - Only determines behavior under static input
 
## □ Each component generates a new, “clean” signal!


- Noise from previous component corrected


 
# Benefits of digital systems




- ❑ Digital components are “restorative”
  - Noise is cancelled at each digital component
  - Very complex designs can be constructed on the abstraction of digital behavior
- ❑ Compare to analog components
  - Noise is accumulated at each component
  - Lay example: Analog television signals! (Before 2000s)
    - Limitation in range, resolution due to transmission noise and noise accumulation
    - Contrary: digital signals use repeaters and buffers to maintain clean signals


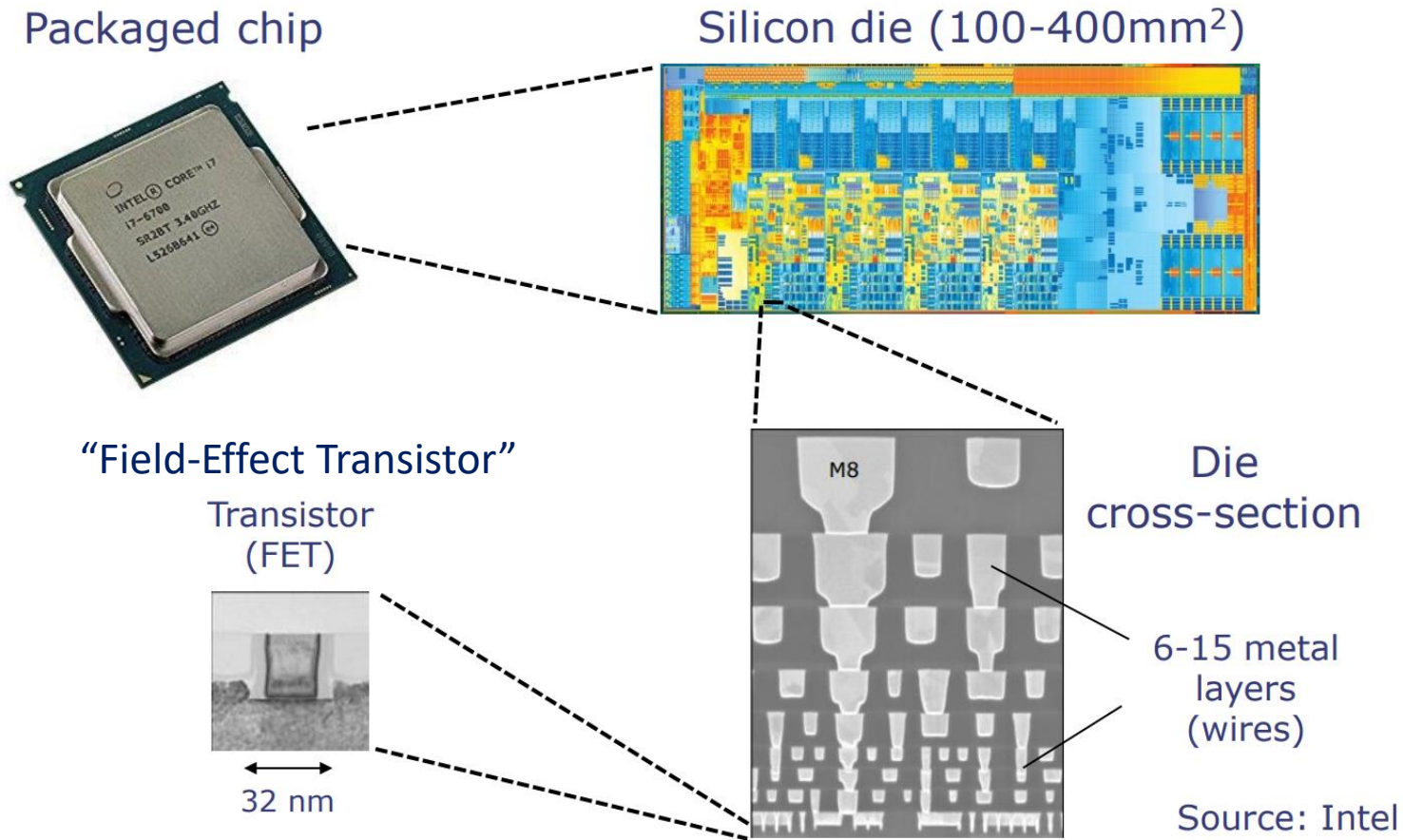
# The basic building block: CMOS transistors



(“Complementary Metal–Oxide–Semiconductor”)




Everything is built as a network of transistors!
  
# The basic building block: CMOS FETs

- Remember CS151 – FETs come in two varieties, and are composed to create Boolean logic




A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

 

CMOS NAND Gate

# Making chips out of transistors...?

 

Intel 4004 Schematics  
drawn by Lajos Kintli and Fred Huettig  
for the Intel 4004 50<sup>th</sup> anniversary project

# The basic building block 2: Standard cell library

## □ Standard cell

- Group of transistor and interconnect structures that provides a boolean logic function

- Inverter, buffer, AND, OR, XOR, ...

- For a specific implementation technology/vendor/etc...
- Also includes physical characteristic information

## □ Eventually, chips designs are expressed as a group of standard cells networked via wires

- Among what is sent to a fab plant

Gate	Delay (ps)	Area ( $\mu^2$ )
<b>Inverter</b>	20	10
<b>Buffer</b>	40	20
<b>AND2</b>	50	25
<b>NAND2</b>	30	15
<b>OR2</b>	55	26
<b>NOR2</b>	35	16
<b>AND4</b>	90	40
<b>NAND4</b>	70	30
<b>OR4</b>	100	42
<b>NOR4</b>	80	32



Example:

Various components have different delays and area!

The actual numbers are not important right now
  
# Aside: Describing chips for foundries

- ❑ GDSII, OASIS file formats
- ❑ Depicts many standard cells connected via multiple wire layers



# CS152: Computer Systems Architecture

## Digital Circuit Design Recap



Sang-Woo Jun

Spring 2023



Large amount of material adapted from MIT 6.004, “Computation Structures”,  
Morgan Kaufmann “Computer Organization and Design: The Hardware/Software Interface: RISC-V Edition”,  
and CS 152 Slides by Isaac Scherson



# Combinational and sequential circuits

❑ Two types of digital circuits

❑ Combinational circuit


○ Output is a function of current input values

- $\text{output} = f(\text{input})$
- Output depends exclusively on input

❑ Sequential circuit

○ Have memory (“state”)

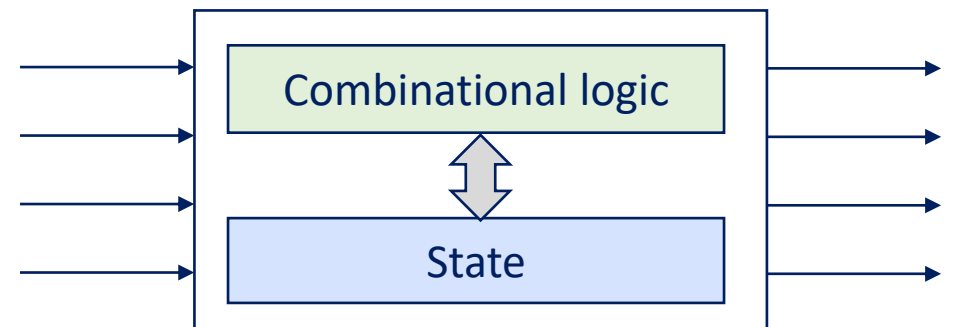- Output depends on the “sequence” of past inputs



# What constitutes combinational circuits

1. Input
2. Output
3. Functional specifications
  - The value of the output depending on the input
  - Defined in many ways!
  - Boolean logic, truth tables, hardware description languages,
4. Timing specifications
  - Given dynamic input, how does the output change over time?


We've done this in CS51/CS151

Hinted at in CS51/CS151

# Timing specifications of combinational circuits
 
## □ Propagation delay ( $t_{PD}$ )

- An upper bound on the delay from valid inputs to valid outputs
- Restricts how fast input can be consumed  
(Too fast input  $\rightarrow$  output cannot change in time, or undefined output)




A good circuit has low  $t_{PD}$   
 $\rightarrow$  Faster input  
 $\rightarrow$  Higher performance

How do we get low  $t_{PD}$ ?

# Timing specifications of combinational circuits

 
## □ Contamination delay ( $t_{CD}$ )

- A lower bound on the delay between input change to output starting to change
  - Does not mean output has stable value!
- Guarantees that output will not change within this timeframe regardless of what happens to input


 
# Back to propagation delay of combinational circuits

- ❑ A chain of logic components has additive delay
  - The “depth” of combinational circuits is important
- ❑ The “critical path” defines the overall propagation delay of a circuit




Critical path of three components  
 $t_{PD} = t_{PD}(\text{xor2}) + t_{PD}(\text{and2}) + t_{PD}(\text{or2})$


Example: A full adder
 
# Sequential circuits

- ❑ Combinational circuits on their own are not very useful
- ❑ Sequential logic has memory (“state”)
  - State acts as input to internal combinational circuit
  - Subset of the combinational circuit output updates state




Abstract model of  
Sequential circuits

 

Slightly more realistic  
Sequential circuit
 
# Synchronous sequential circuits

- ❑ “Synchronous”: all operations are aligned to a shared clock signal
  - Speed of the circuit determined by the delay of its longest critical path
  - For correct operation, all paths must be shorter than clock speed
  - Either simplify logic, or reduce clock speed!



# Timing constraints of state elements


- ❑ Synchronous state elements also add timing complexities
  - Beyond propagation delay and contamination delay
- ❑ Propagation delay ( $t_{PD}$ ) of state elements
  - Rising edge of the clock to valid output from state element
- ❑ Contamination delay ( $t_{CD}$ )
  - State element output should not change for  $t_{CD}$  after clock change
- ❑ Setup time ( $t_{SETUP}$ )
  - State element should have held correct data for  $t_{SETUP}$  before clock edge
- ❑ Hold time ( $t_{HOLD}$ )
  - Input to state element should hold correct data for  $t_{HOLD}$  after clock edge



# Timing behavior of state elements
 
## □ Meeting the setup time constraint

- “Processing must fit in clock cycle”
- After rising clock edge,
- $t_{pD}(\text{State element 1}) + t_{pD}(\text{Combinational logic}) + t_{\text{SETUP}}(\text{State element 2})$
- must be **smaller** than the clock period




Otherwise, “timing violation”



# Timing behavior of state elements
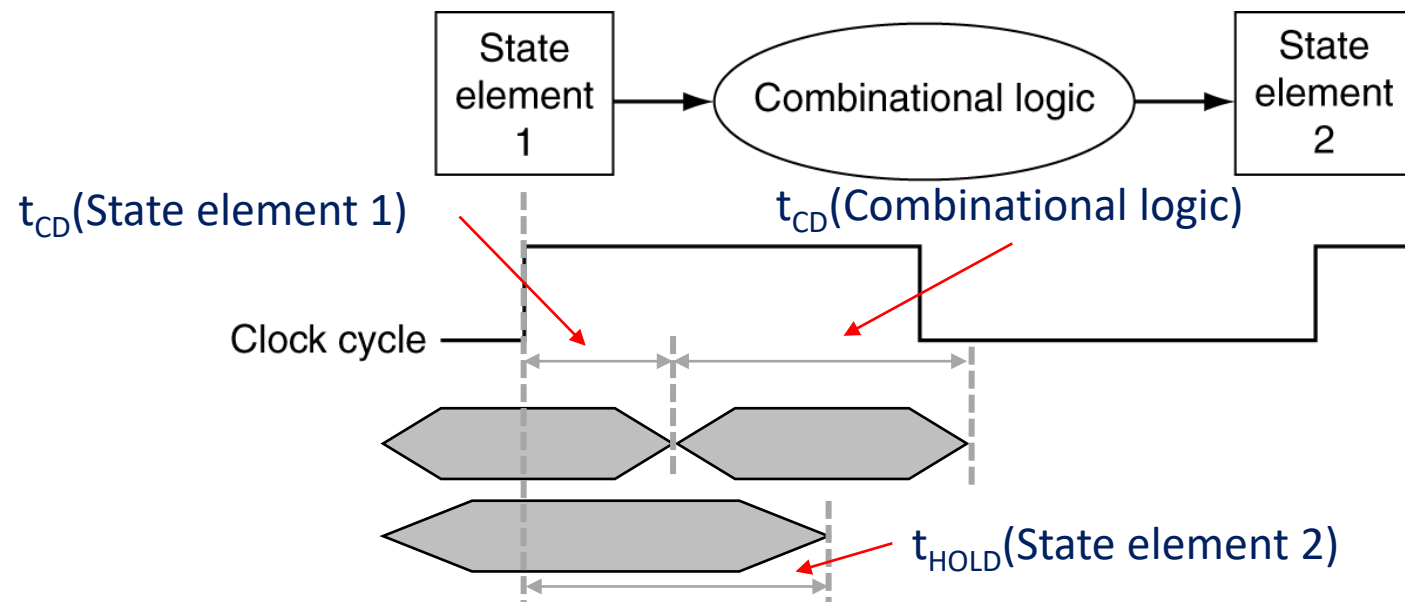
## □ Meeting the hold time constraint

- “Processing should not effect next state too early”
- After rising clock edge,
- $t_{CD}(\text{State element 1}) + t_{CD}(\text{Combinational logic}) = \text{Guaranteed time output will not change}$
- must be **larger** than  $t_{\text{HOLD}}(\text{State element 2})$



# Setup and hold time window

  

If any constraint is violated, state may hold wrong data!

# Real-world implications

- ❑ Constraints are met via Computer-Aided Design (CAD) tools
  - Cannot do by hand!
  - Given a high-level representation of function, CAD tools will try to create a physical circuit representation that meets all constraints
- ❑ Rule of thumb: Meeting **hold time** is typically not difficult
  - e.g., Adding a bunch of buffers can add enough  $t_{CD}$  (Sequential Circuit)
- ❑ Rule of thumb: Meeting **setup time** is often difficult
  - Somehow construct shorter critical paths, or
  - reduce clock speed (We want to avoid this!)

How do we create shorter critical paths for the same function?

# Simplified introduction to placement/routing


- ❑ Mapping state elements and combinational circuits to limited chip space
  - Also done via CAD tools
  - May add significant propagation delay to combinational circuits

## ❑ Example:

- Complex combinational circuits 1 and 2 accessing state A
- Spatial constraints push combinational circuit 4 far from state A
- Path from B to A via 4 is now very long!


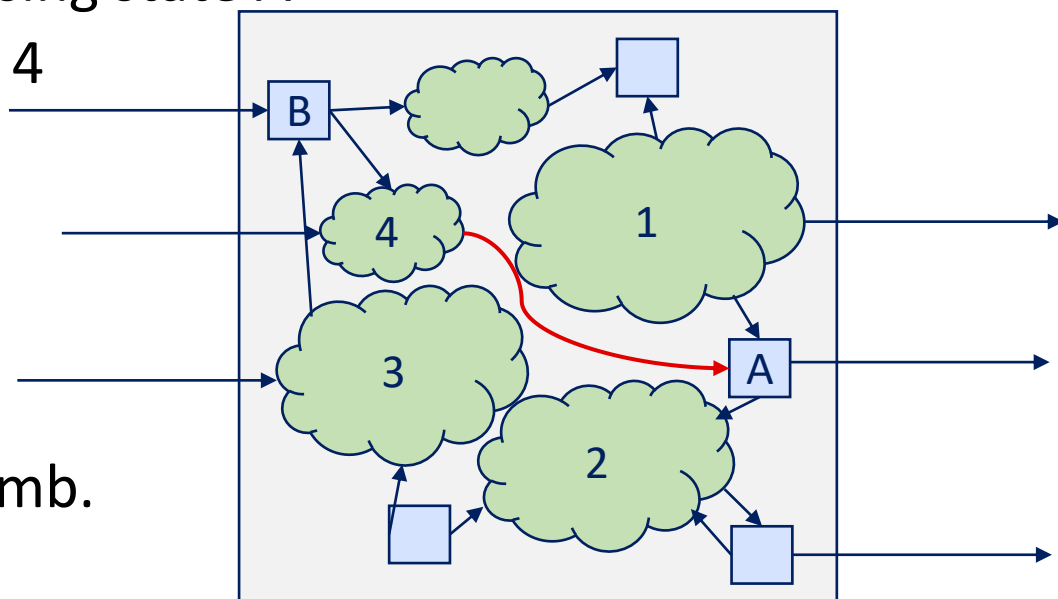
## ❑ Rule of thumb:

- One comb. should not access too many state
- One state should not be used by too many comb.


  
# Looking back: Why are register files small?

- Why are register files 32-element? Why not 1024 or more?



Hierarchical design of a  
8x1 multiplexer

Propagation delay increases with more registers!

# Real-world example

- ❑ Back in 2002 (When frequency scaling was going strong, but larger FETs)
  - Very high frequency (multi-GHz) meant:
  - ... setup time constraint could tolerate
  - ... up to 8 inverters in its critical path
  - Such stringent restrictions!

Can we even fit a 32-bit adder there? No!